


CSULB  
CECS225  
Lab ALU

**OBJECTIVE:** Create an 8-bit ALU (Arithmetic Logic Unit).

**PROCEDURE:** First make sure you have the halfadder, fulladder, ripplecarry4, ripplecarry8, and ripplesubtractor8 module source files from the previous labs.

Be sure to use the **exact same file names** that were specified in the previous two labs.

 
Now create an 8-bit AND gate according to the block diagram below:



Name the file **and8.v** and use the module skeleton below to get started:

```
module and8(  
    input [7:0] a, b,  
    output [7:0] y  
);  
    and  
        a0(y[0], a[0],    ),  
        a1(y[1], a[1],    ),  
        a2(  
  
  
  
  
  
  
  
  
        a7(y[7],    , b[7]);  
endmodule
```

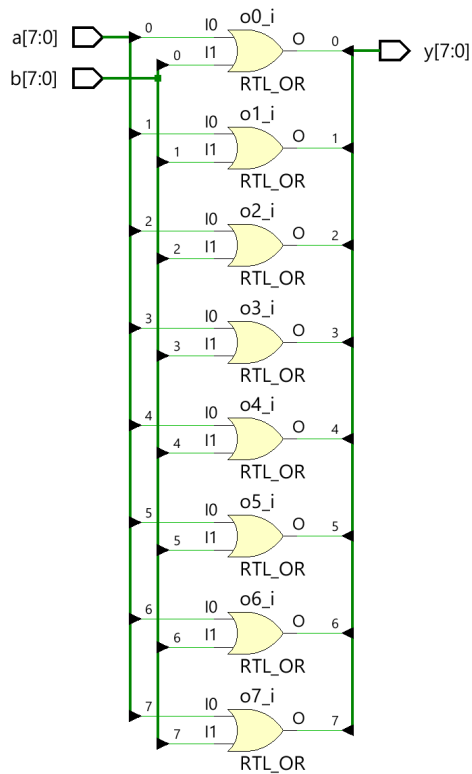Then create an 8-bit OR gate according to the block diagram below:




The following module will be given for you to use:

Create **slt8.v** given the Verilog source code below:

```
module slt8(
    input [7:0] a, b,
    output reg [7:0] y
);
    always @(*)
    begin
        if (a < b)
            y = 8'b0000_0001;
        else
            y = 8'b0000_0000;
        end
    endmodule
```

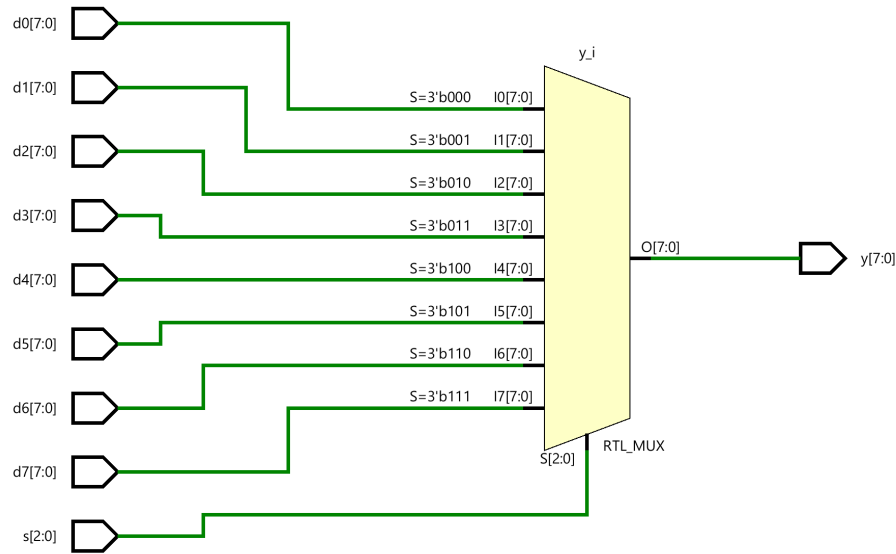Create **mux8to1\_8bit.v** given the Verilog schematic below:




```

module mux8(
    input [7:0] d0, d1, d2, d3, d4, d5, d6, d7,
    input [2:0] s,
    output reg [7:0] y
);
always @(*) begin
    case (s)    //begin
        3'b000: y =d0;


        3'b111: y =d7;
        default: y = 8'bx; //invalid output by default
    endcase
end
endmodule

```

 Create the Arithmetic Logic Unit Block diagram below:



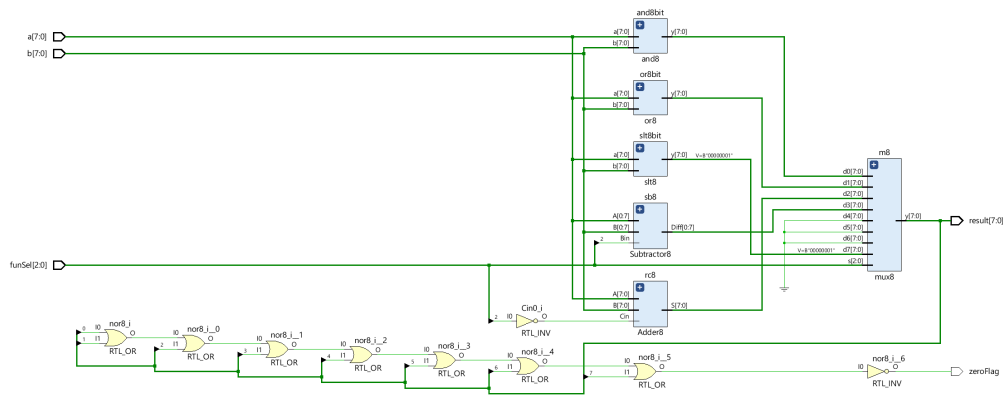Which should give you the following schematic:



Name your Verilog source file as **alu8.v**, a skeleton is shown below:

```

module alu8(
    input [2:0] funSel,
    input [7:0] a, b,
    output zeroFlag,
    output [7:0] result
);

    wire [7:0] andab, orab, addab, subab, slthb;

    and8 and8bit (a, b, andab);
    or8 or8bit (a, b, orab);
    Adder8 rc8(1'b0, a, b, addab,); //leave the last space after the, empty
    Subtractor8 sb8(, a, b, subab,); //leave the last space after the, empty
    slt8 slt8bit (, , slthb);
    mux8 m8(andab, orab, addab, subab, slthb, 8'bx, 8'bx,8'bx, zeroFlag, funSel, result);

    nor nor8(zeroFlag, result[0], result[1], result[2], result[3], result[4], result[5],
             result[6],result[7]);

endmodule

```

Source code for testbench.sv is provided below:

```

module TestBench();
    reg [7:0] a, b;
    reg [2:0] funSel;
    wire [7:0] result;
    wire zero;

    integer i;
    alu8 uut(funSel,a, b, zero, result);
    initial begin
        b = 8'b00001111;
        a = 8'b01011010;
        for(i=0; i< 8; i = i + 1)
            begin
                funSel = i;
                test_case;
            end //for
        b = 8'b00001111;
        a = 8'b01011010;
        test_case;    //one more test case
        $finish;
    end //initial

    task test_case;
    begin
        #1;
        case (i)
            3'b000: $display("\nTesting the AND function");
            3'b001: $display("\nTesting the OR function");
            3'b010: $display("\nTesting the Addition function");
            3'b110: $display("\nTesting the Subtraction function");
            3'b111: $display("\nTesting the Set Less Than function");
            default: $display("\nInvalid function Selection Code");
        endcase
        if (i== 2)
            i = 5;

        $display("a = %b, b = %b, result = %b, zero = %b", a, b, result, zero);
    end //test_case
endtask
endmodule

```

If everything works correctly then the following console output will be produced:

```

Testing the AND function
a = 01011010, b = 00001111, result = 00001010, zero=0

Testing the OR function
a = 01011010, b = 00001111, result = 01011111, zero=0

Testing Addition
a = 01011010, b = 00001111, result = 01101001, zero=0

Testing Subtraction
a = 01011010, b = 00001111, result = 01001011, zero=0

Testing Set Less Than Function
a = 01011010, b = 00001111, result = 00000000, zero=1

Testing Set Less Than Function
a = 00001111, b = 01011010, result = 00000001, zero=0

```

If your module did not work correctly CHECK your code again then ask for help

**WHAT TO TURN IN:** Once the modules in this lab are working correctly:

- Copy the contents of your modules to a word document, a screenshot of the timing diagram and output in the console, and a link to video showing a screen recording of your while explaining it and showing a simulation running. Save as a pdf and upload to the beachboard dropbox.

**NOTE: `always@(*)`** is just a shortcut for listing all of the wires that the always block depends on.

An incomplete event\_expression list of an event control is a common source of bugs in register transfer level (RTL) simulations. The implicit event\_expression, `@*`, is a convenient shorthand that eliminates these problems by adding all nets and variables that are read by the statement (which can be a statement group) of a procedural\_timing\_control\_statement to the event\_expression.

**Extra Credit:**

As you can tell we still have room for 3 more operations in this ALU. Add one extra operation of your choice using any of the non-used selection, with all the needed files and testbench modification for an extra 5 points.

If you add three more instructions correctly with all the needed modifications, correct outputs simulation and demonstration, this is 10 more points.