
 


CSULB  
CECS225  
Lab Mux

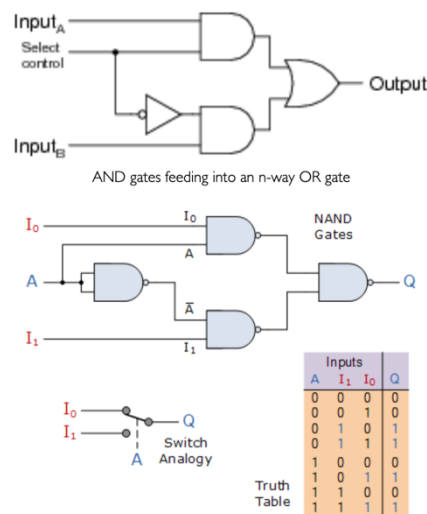In general, the MUX is looks like the image, as a high-level abstraction:  
The image shows the analog design, it selects between multiple input signals.



This is the digital design of the multiplexer



Verilog Implementation:

We can use the assign operator with the expression that is a direct Verilog equation, we can use a set of Use set of predefined primitives (simple gate-level function blocks).  
Or we can use the followings:

you need to put it inside a module. (I recommend that you understand and try each implementation using Vivado)

```

wire in0, in1, sel, out;
wire [1:0] out=(sel)?in1:in0;

```

```

wire in0, in1, sel, out;
d = {in0, in1};
out = d[sel];

```

The main issue is when you go to larger numbers of inputs, like 4, 8, 16, 32.

Another good option is the *case* statement, which is extremely useful in module format:

```
module (in0, in1, in2, in3, in4, in5, in6, in7, sel, out);

input [63:0] in0, in1, in2, in3, in4, in5, in6, in7; [2:0] sel;
input [2:0] sel;
output[63:0] out;

always @(in0 or in1 or in2 or in3 or in4 or in5 or in6 or in7 or sel)

    case (sel)

        3'b000 : out = in0;
        3'b001 : out = in1;
        3'b010 : out = in2;
        3'b011 : out = in3;
        3'b100 : out = in4;
        3'b101 : out = in5;
        3'b110 : out = in6;
        3'b111 : out = in7;

    endcase

endmodule
```

**For this lab**  
**Design a 2-to-1 mux.**

```
module mux2to1();
input a, b, sel;
output y;

//1- use
// assign [signal_name] = [expression];

//2- Use set of predefined primitives (simple gate-level function blocks)
//to define your mux2to1.

//3- Try all previous implementations

//4- use a simple testbench to test the 2-to-1 mux and to make sure it is
working fine -generate the time line and output the truth table using the
$display statement
```

When you **try a new implementation comment the previous one to have** one implementation only in the design.

**5- Design a 4-to-1 mux by cascading 2-to-1 muxes. Use testbench at the end of this document**  
**6- Then design an 8-to-1 mux by cascading the 4-to-1 mux (for the last one you have to modify the testbench as well)**

This is the testbench for 4 to 1 multiplexer. Make sure to fill in the lines that say “**your module name here**” or “**your input x here**”, etc. with the correct port name in your 4:1 mux module.

```
module mux4to1tester;
    reg d3, d2, d1, d0, s1, s0;
    wire y;

    "your module name here" dut(. "your input 0 name" (d0),
                                . "your input 1 name" (d1),
                                . "your input 2 name" (d2),
                                . "your input 3 name" (d3),
                                . "your select bit 0 name" (s0),
                                . "your select bit 1 name" (s1),
                                . "your output name" (y));

    integer i;

    initial begin
        $display("Mux 4 to 1 tester!");
        d0 = 1'b1; d1= 1'b0;
        d2 = 1'bx; d3= 1'b1;
        $display("\tTest case\t d3\t d2\t d1\t d0\t s1\t s0\t | \ty");
        for(i = 0; i<4; i = i + 1)
            begin
                {s1,s0} = i;
                #1 $display("%d\t\t %b\t %b\t %b\t %b\t | \t %b", i, d3, d2, d1, d0, s1, s0, y);
            end
        $finish;
    end
endmodule
```

Please submit a copy of your code and a link to a video explaining your code