 


Model a ripple carry adder and review module instantiation.


**PROCEDURE:** First create the half adder using an XOR gate and an AND gate.



1. Complete the skeleton below to create the Half Adder Verilog module:


```
module HalfAdder(
    input a,
    input b,
    output c,
    output s
);
    xor x1(
        );
    and a1(
        );
endmodule
```

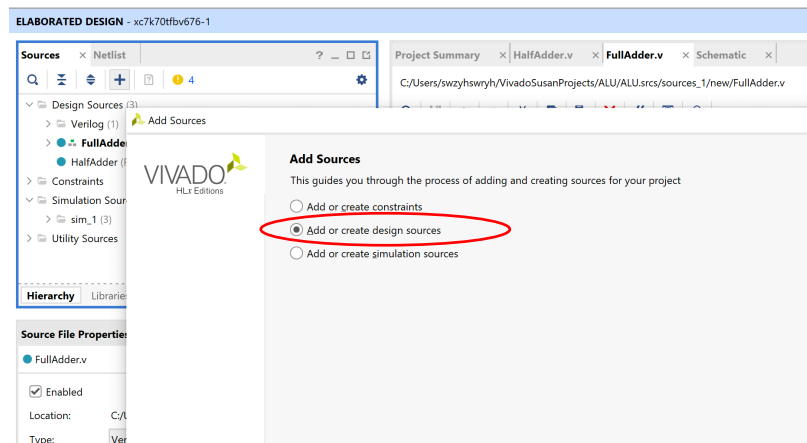2. From the Flow Navigator, click add Sources and add another design file. Or click the + button to create a new file, enter the name **FullAdder.v** as shown below




Before the module definition in the new file include the following line

**``include "HalfAdder.v"`**

 

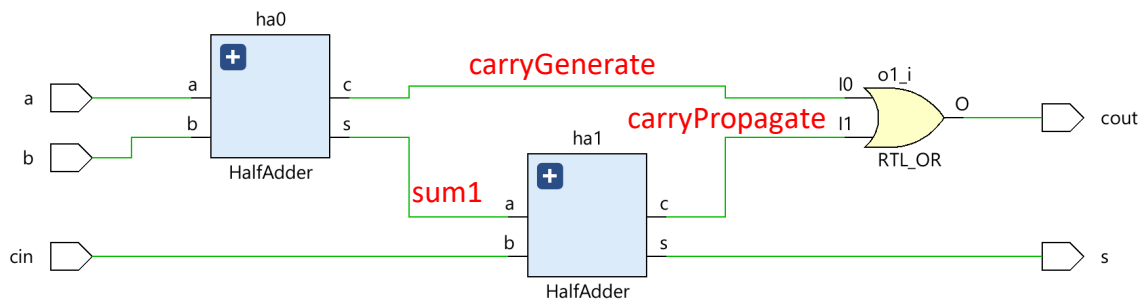Then finish the fullAdder module according to the circuit depicted below, observe the interconnections:



```

21 |
22 | `include "HalfAdder.v"
23 |
24 | module FullAdder(
25 |     input a,
26 |     input b,
27 |     input cin,
28 |     output s,
29 |     output cout
30 | );
31 |     wire carryGenerate, carryPropagate, sum1;
32 |     HalfAdder
33 |         ha0(
34 |             a,
35 |             b,
36 |             s,
37 |             c
38 |         );
39 |     HalfAdder
40 |         ha1(
41 |             cin,
42 |             s,
43 |             sum1,
44 |             cout
45 |         );
46 |     RTL_OR
47 |         o1(
48 |             carryGenerate,
49 |             carryPropagate,
50 |             cout
51 |         );
52 | endmodule

```

**Explanation:** the **include** directive copies the source code from **HalfAdder.v** into **FullAdder.v** so that the **HalfAdder** module can be “instantiated” or used.


The **halfadder** module instantiation occurs on lines 32, 33, and 34 of **FullAdder.v**. The **HalfAdder** module is called by name on line 32, *two instances* are created on lines 33 and 34.

Module instantiation works just like using gate level primitives except the order of inputs and outputs may vary.


The **HalfAdder** port list is (**input a, input b, output c, output s**) so variables must be put on the **HalfAdder** instance port list in the order that is determined by the **HalfAdder** module definition.

The Ripple Carry Adder (**RippleCarry4**) will be the **top level module** for this lab. A **top level** module can be thought of as a main function. In Verilog the top level module is at the top of the hierarchy i.e. it typically contains all of the sub modules in a project/design.

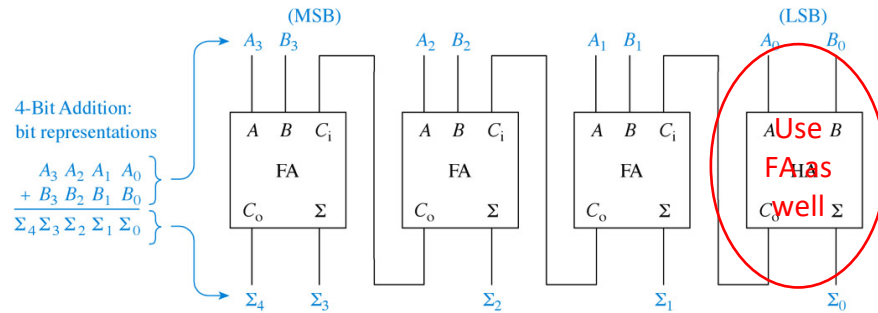
- Complete the module skeleton that is given below according to the block diagram **but use a full adder for the LSB instead of HA:**



This is how you declare vectors (buses)

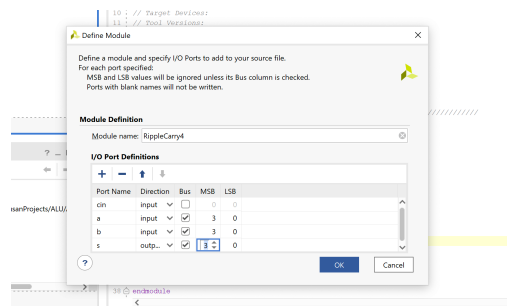

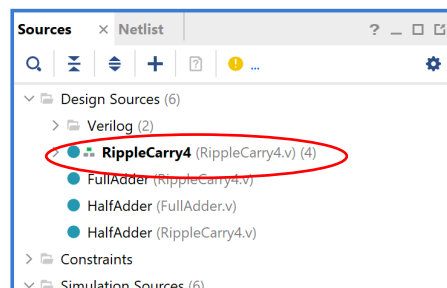Notice, when you synthesis how your last module will automatically become the **top level module** (It will be recognized as the contents of **design.sv**)



```
`include "FullAdder.v"
module RippleCarry4(
    input cin,
    input [3:0] a,
    input [3:0] b,
    output [3:0] s,
    output cout
);
```

```
    wire cout0, cout1, cout2;
```

```
    FullAdder
    fa0(a[0],      , cin, s[0], cout0 ),
    fa1(      , b[1],      , s[1], cout1),
    fa2(a[2],      , cout1,      ,      ),
    fa3(      ,      ,      ,      ,      );
```

```
endmodule
```

Once the RippleCarry4 module has been completed, it is time to test the design. Testbench code is given below:

```

1  timescale 1ns / 1ps
2  ///////////////////////////////////////////////////////////////////
3  //
4  // Name: Susan Nachawati
5  //
6  // Create Date: 10/26/2020 01:38:07 PM
7  // Design Name: RippleCarry4
8  // Module Name: TestBench
9  //
10 //
11 ///////////////////////////////////////////////////////////////////
12
13
14 module TestBench();
15     reg cin;
16     reg [3:0] a, b;
17     wire [3:0] s;
18     wire cout;
19
20     RippleCarry4 rut(cin, a, b, s, cout);
21
22     integer i;
23     initial
24     begin
25         $display ("4-bit Ripple Carry");
26
27         cin = 0;
28         for(i=0; i <8; i = i+1)
29             begin
30                 #1 {a, b} = $random;
31                 #5 $display("a = %d, b = %d, s = %d, cout = %b", a, b, s, cout);
32             end //for
33     end//initial
34 endmodule
35

```

If everything works correctly then the following console output will be produced:


#### 4-bit Ripple Carry

```

a = 2, b= 4, s = 6, cout = 0
a = 8, b= 1, s = 9, cout = 0
a = 0, b= 9, s = 9, cout = 0
a = 6, b= 3, s = 9, cout = 0
a = 0, b= 13, s = 13, cout = 0
a = 8, b= 13, s = 5, cout = 1
a = 6, b= 5, s = 11, cout = 0
a = 1, b= 2, s = 3, cout = 0

```

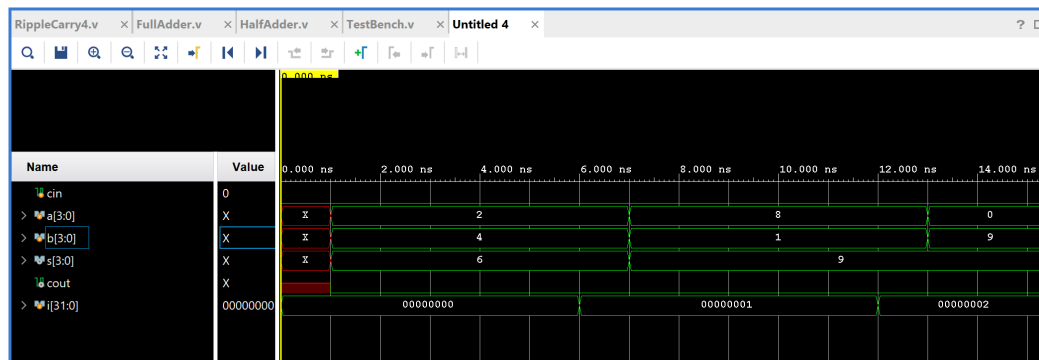And your timing diagram should look like this:



If your module did not work correctly get assistance from the instructor or a reputable student to troubleshoot your design.

**WHAT TO TURN IN:** Once your RippleCarry4 module is working correctly:

- Copy the contents of your **RippleCarry4** module to a file named with a screenshot of your output and timeline.
- Explain your briefly while voice recording your screen, simulate your code, show the timeline being generated, and the output explain your output. Upload to YouTube.
- Save a link to your video in the same file as your code and the output. Upload as a pdf.

**NOTE:**

Keep the source files from this lab as they will be used in future Labs!  
halfadder, fulladder, and RippleCarry4 modules will be used in upcoming labs.